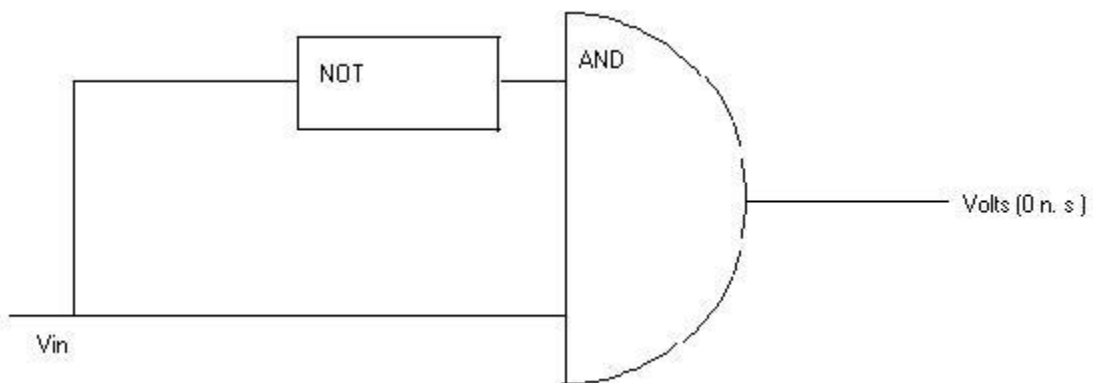


## TATA ELXSI PAPERS HELD AT DRIEMS ,CUTTACK ON 24th APRIL 2004

There were two rounds 1)TECH(30 ques,30 mins)2)APTITUDE(30 ques,30 mins)

### TECH QUESTIONS (Electronics & TC)

- CMRR is given=  
Differential gain is given= NOT  
Inputs:  
+ve end=2v,-ve end=1v of the OP-AMP  
Find the output voltage?
- CRO is in X-Y mode.Sinusoidal inputs have 90degrees phase difference between them. What will appear on the display? a)circle b)line c)ellipse d)triangular wave
- Which has least propagation delay?  
a)ECL b)TTL c)RTL d)CMOS
- In a ripple counter how many change in states happen when count changes from 7 to 8?  
a)1 b)2 c)3 d)4
- Max. no. of variables that can be represented in K-MAP?  
a)3 b)5 c)7 d)none of these
- How many comparators are required in a n-bit flash ADC?  
a) $2^{(n-1)}$  b) $(2^n)-1$  c) $2^n$  d) n
- What is an EEPROM?  
a)Programmable transistor  
b)Transistor  
c)SRAM  
d)
- Time period of input voltage=8ns. / Find the duty cycle of Vout.




Voltage across one capacitor is V volts. Another capacitor is added at its one end(now the two are in series). What is the voltage across their ends?

- a)V b) $V/2$  c)2v d)none of these
- In an SCR why silicon is used?  
a) available easily

- b) has much less reverse saturation current than Germanium
- c) has greater reverse sat.current than Ge
- d)


10. Output=?

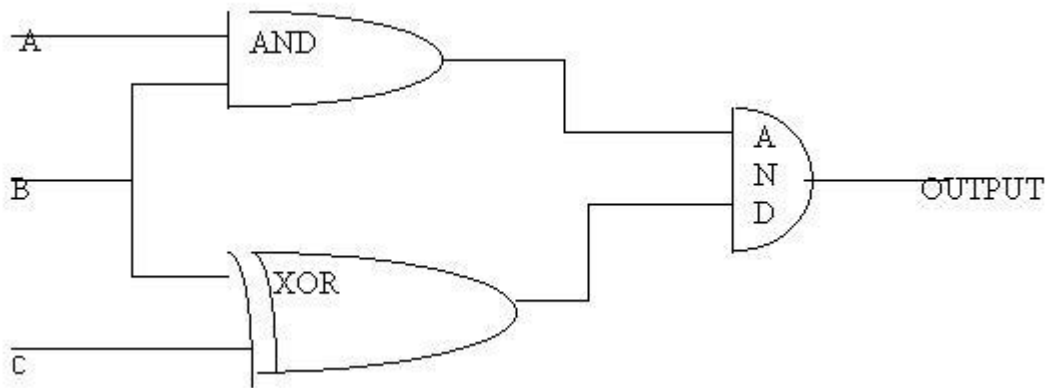

- a)  $A'+B'+C$
- b)  $A+B+C'$
- c)  $A(B'+C')$
- d)  $B'+C'+A'$


11. There was a question using transmission gates. Three inputs were A,B,C. Answer was  $(A+B \text{ xor } C)$

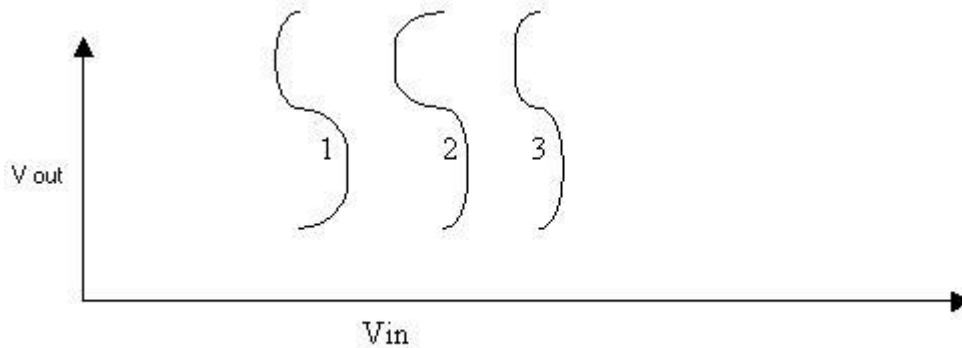12. How to get the characteristic figure changed from 1 to 3?(characteristic diagram)



- a) By increasing gate width of NMOS
- b) -----do----- of CMOS
- c) By increasing gate voltage

14. Find propagation delay?

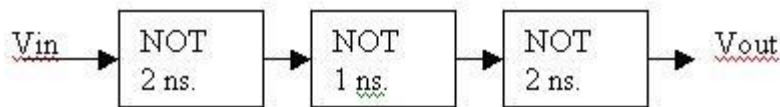


- a) 200Hz
- b) 150Hz
- c) 5Hz
- d) 2Hz

15. A diagram was given to identify?


- a) Synchronous counter

- b)Ripple counter
  - c)Shift register
  - d)None of the above
- answer was sync. Counter


16. Find  $V_a$  and  $I_a, I_b$ ?

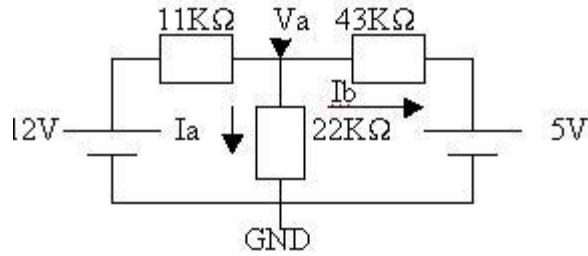

17. Find ammeter current  $I_a$ ?

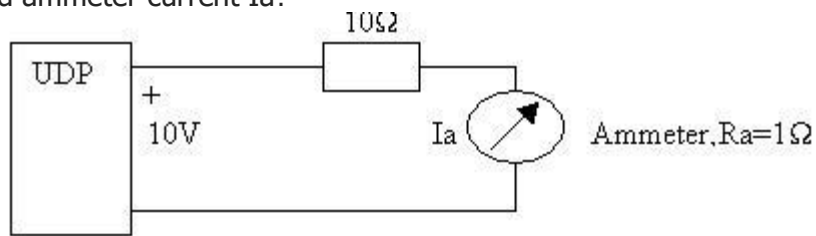

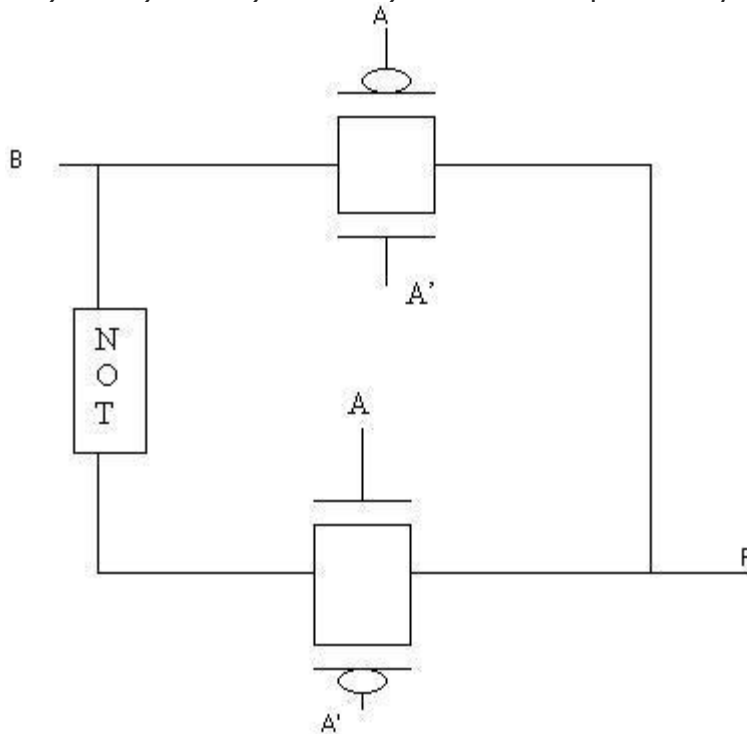- a)10V b)9.09V c)11.01V d)0.9V these options may be wrong.




18.


This acts as a:

- a)OR
- b)XOR
- c)AND
- d)NOR





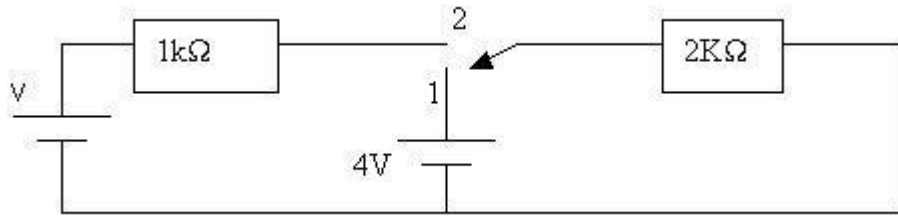
19. At  $t=0$  if position is changed from 1 to 2, find the voltage across  $1\text{k}\Omega$ ?



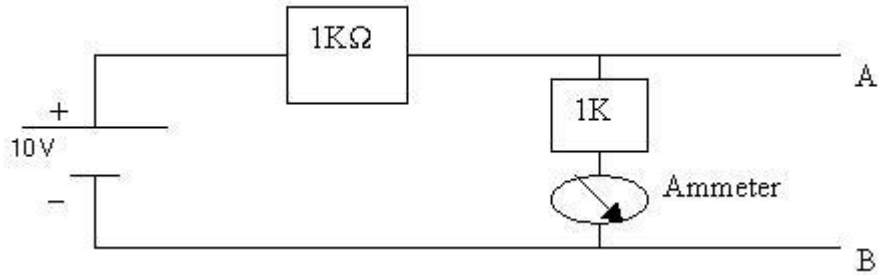- a) 4V b) 2V c) 1.5V d) none of these
20. Find thevenin voltage and resistance across A and B




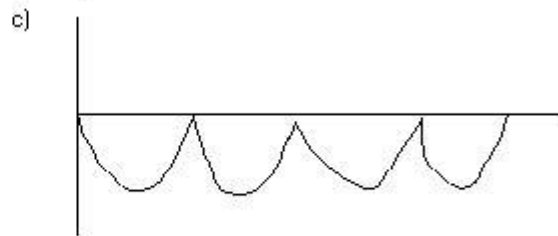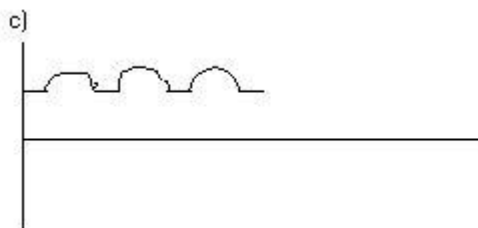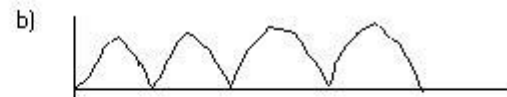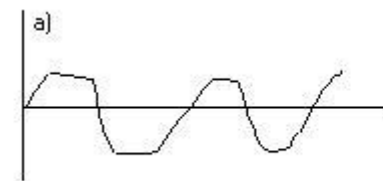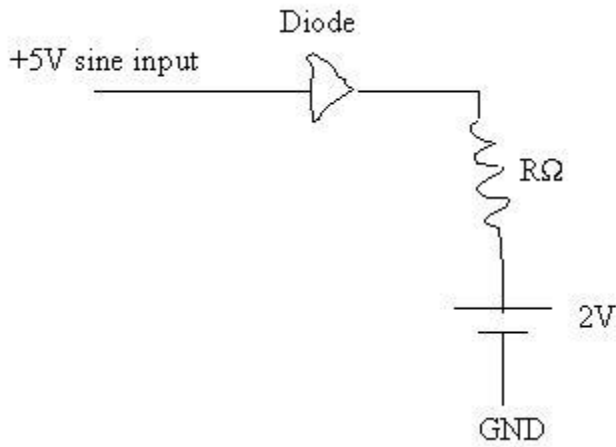21. how will be the output voltage across R ?




Ans C

22. What is this ?

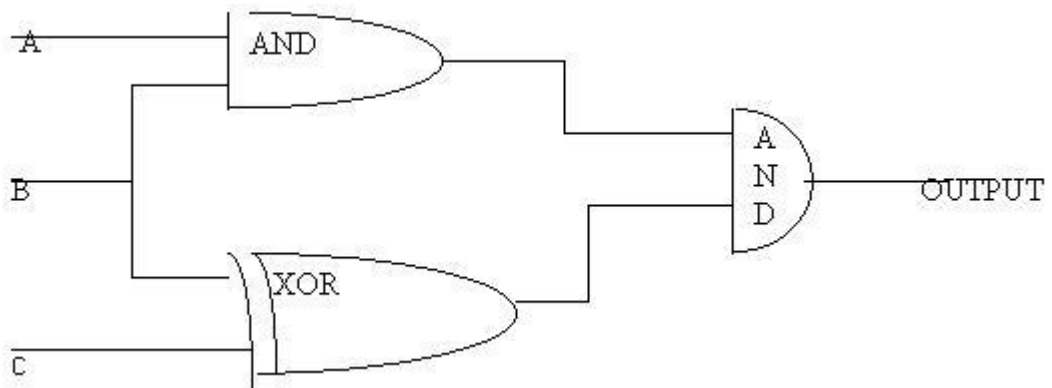

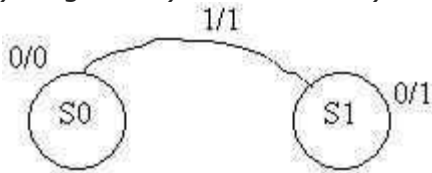
a)Integrator b)Differentiator c)Antilog differentiator d)Log differentiator



23.



Flip-flop state diagram question. What does the above represent?

24. What is this?

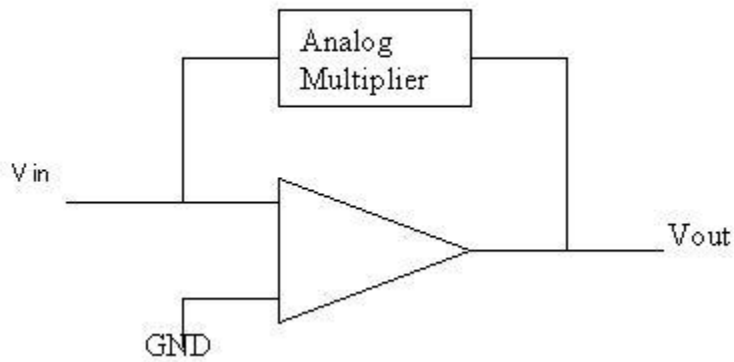


a)Squaring device b)Divider c)Square root ckt d)

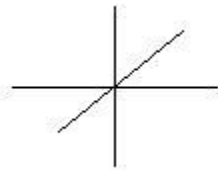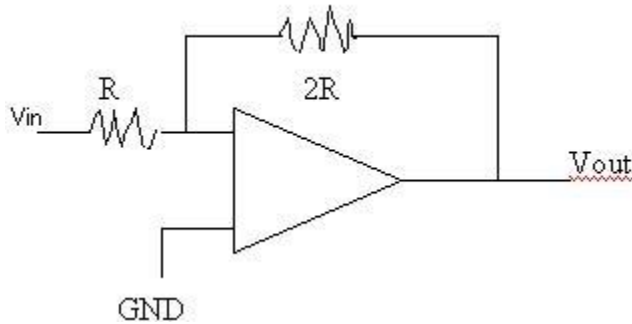25. How will be the output vs. input graph if  $V_{in}=10V$ , sat voltage of OP-amp is  $14V$ ?




26. Basic memory cell of dynamic RAM a. Capacitance  
 b. Flip flop  
 c. Transistor  
 d. Transistor with Capacitor
27. Ideal Power Supply has  
 a. Zero internal resistance  
 b. High O/P resistance  
 c. High I/P resistance Freshersworld.com  
 d. Low O/P resistance
28. Which type of transmission line will have max. value of characteristic impedance  
 a. Open Wire line b. Coaxial Cable  
 c. Twin lead line d. None
29. For same peak value of current, which waveform will have least RMS value a. Sine b. Square  
 c. Triangular  
 d. Full wave rectified wave
30. -V analogy displacement is analogous to  
 a. Voltage b. Conductance  
 c. Magnetic Flux Linkage  
 d. Capacitance
- Similarly.....In F-I analogy displacement is analogous to  
 a. Charge  
 b. Resistance Freshersworld.com  
 c. Inductance  
 d. Current

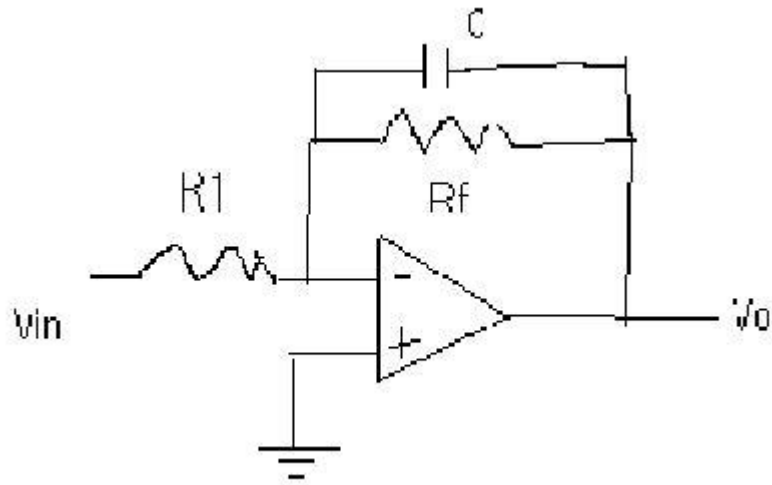31. In the following circuit  $V_o/V_{in} =$  (there were 4 options)




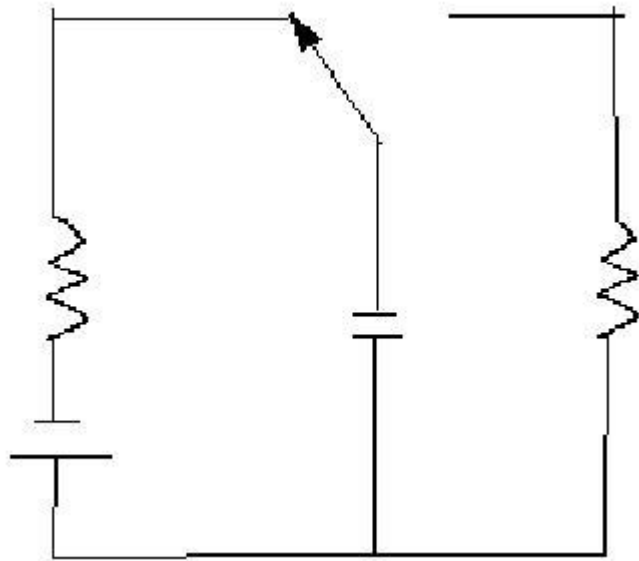32. In the following circuit the charging and discharging time is (i don't remember the options)



Don't remember the other value of other res and cap .But some values are given

33. The output at X acts as....

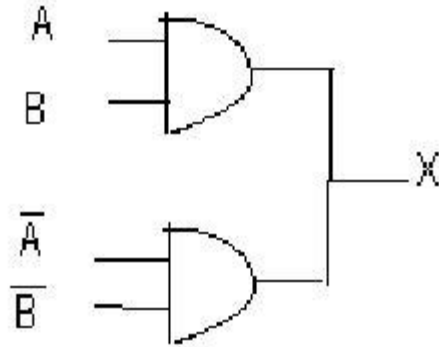

- a. OR gate
- b. AND gate
- c. XOR gate
- d. XNOR gate

34. The CRO in X-Y mode gives the following figure. If signal applied to the Y-plate is  $2\sin(\omega t)$  then the signal applied to the X is a.  $2\sin(\omega t)$  b.  $2\sin(\omega t + \pi/4)$  c.  $2\sin(\omega t)$  d.  $2\sqrt{2}\sin(\omega t + \pi/4)$

