

TataElxsi hardware paper

- (1).problem on lissajous pattern: in x-y mode if v_x applied to x-axis is $2 \sin \omega t$ then what is the v_y to be applied to y-axis so that we observe the following pattern on the cro : [angle b/n x-axis and the diagonal line is 45degrees] ans is $2\sqrt{2} \sin (\omega t +45)$
- (2)what is the resolution of an adc : $v_{ref}/(2^{pow n})$.
- (3)some circuit is given with two f/f s ,what is that circuit? Ans may be shift reg
- (4)spatial to temporal converter is ? (a) shift reg (b) counter (c) adc ans may be adc
- (5) darlington is used for _____ ans high current gain
- (6)some circuit with nand gates is given ,what is that circuit ans is xor
- (7) a wired circuit with some nand gates is given asked the function of that circuit
- (8) an opamp circuit is given asked to find the transfer function of it (I think its an ideal integrator circuit)
- (9)a pole zero pattern of an impedance function is given . it has a conjugate pair of zeros and a conjugate pair of poles ,then what elements does the impedance consists of? Ans LC elements
- (10)most computers wont use floating point arithmetic .why?
a.costly b. slow c. cant
- (11)bit-slice processor mean ans used for shift ,masking of bits
- (12)ac motor used in servo applications is (a) single phase induction b.2 phase induction c. 3 phase induction
- (13)tv resolution depends on a. bandwidth 2. detector c. no. of frames /sec
- (14)equalizing pulses are sent in tv during a. horizontal blanking b. vertical blanking
- (15)cdma is not suitable for satellite communication . why ? ans may be complexity of operation
- (16)given some waveforms and asked that which of the waveforms will have odd harmonics of sine terms
- (17)asked for two's complement of a number
- (18)maximum signed no. represented by a 8 bit computer
- (19)a chip has a capacity of 256bits,to implement a 1KB capacity how many chips are required
ans 32

(20) ecl operates in ____ and ____ regions of the transistor

(21) given a transient circuit ,asked for time constant while charging and discharging

(22) he had given 4 statements about a f/f and asked which of them are correct

1. it can store a bit 2. jk f/f have race when storing a 2 bit info 3. master slave is used to store a 2 bit info

4. d f/f used as a latch for multiplexing operations

(23) Venn diagram is given and asked to write expression for the shared portion in it

(24) cb and ce are ____ biased when transistor is in saturation

(25) condition for nyquist rate .

(26) carry look ahead adder is 1.fast 2. requires more h/w 3. costly

(27) ideal power supply will have a. zero internal resistance b. more o/p resistance c. less o/p resistance

(28) a problem on cro and probe interface i.e design of an attenuator for the cro probe
(formula for it is $R_1 * c_1 = R_2 * C_2$)